

| | | |
|-------------------------|--|-------------------|
| Course: CSE 251 | Course Title: Electronic Circuits | Section: 5 |
| Date: 27/11/2021 | Name: | ID: |

Q) Determine V_o and i_o in the circuit below.

[Marks: 10]

