

**Department of Computer Science & Engineering**  
**CSE 251– Electronic Circuits**  
**Semester Final Exam**

**Course Code:** CSE 251  
**Teacher's Initial:** SMRC  
**Time:** 90 Mins

**Semester:** FL 21  
**Section:** 5 (Five)  
**Full Marks:** 50

All the questions must be answered. Symbols have their usual meanings.

**Question 1**

[CO<sub>1</sub>, 20]

Determine the drain current ( $I_D$ ), gate-source voltage ( $V_{GS}$ ) and the drain-source voltage ( $V_{DS}$ ) at the Q-point of the following circuits. Also mention their operational modes (linear/saturation). [Given for both MOSFETs,  $V_{TH} = 0.75V$  and  $\mu_n C_{ox} W/L = 1.28 \text{ mA/V}^2$ . Ignore the short channel effect.]

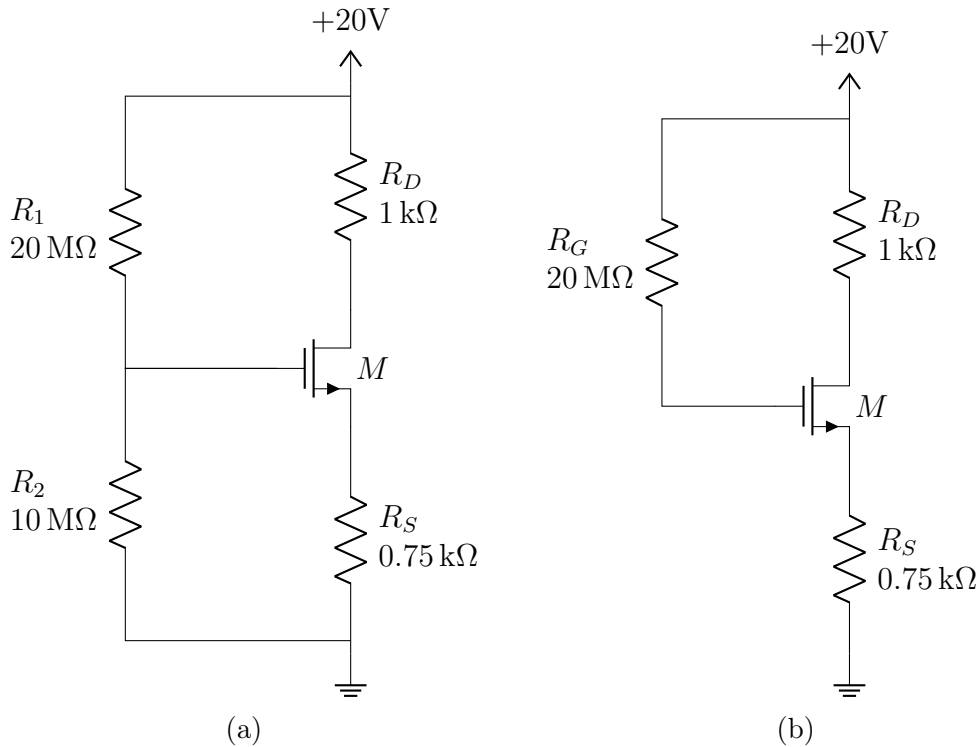


Figure Q.1: Circuit Diagrams for Question-1.

**Question 2**

[CO<sub>2</sub>, 15]

Choose a suitable bias circuit working in saturation mode from Figure Q.1, along with the associated Q-point values. Draw a Source Follower amplifier configuration by connecting proper input and output terminals to the bias circuit. Now determine,  $g_m$ ,  $Z_{in}$ ,  $Z_{out}$ ,  $A_{v0}$ ,  $A_v$ ,  $G_v$  and  $v_{out}$  of the Source Follower circuit. [Take, input source,  $v_{sig} = 1.5V$  peak sinusoid, source impedance,  $R_{sig} = 888 \text{ k}\Omega$ , load impedance,  $R_L = 0.8 \text{ k}\Omega$  and the CLM parameter,  $\lambda = 25 \mu\text{S}$ ]

**Question 3**[CO<sub>2</sub>, 7]

Using the small signal model of MOSFET, derive the expression of the input impedance ( $Z_{in}$ ) of the following amplifier circuit.

 


Figure Q.3: Circuit Diagram for Question-3.

**Question 4**[CO<sub>2</sub>, 8]

Design CMOS logic circuit for the logic function,  $F(x, y, z) = \overline{x + y \cdot z}$