

Course: CSE 251 – Electronic Circuits, Section-5
Instructor: Surajit Das Barman, Senior Lecturer, CSE Department
Full Marks: 20
Time: 1 Hour and 25 Minutes

Note: There are FIVE questions, answer ALL of them. Course outcomes (CO), cognitive levels and marks of each question are mentioned at the right margin.

1. **Determine** the output current i_o for the circuit in Fig. 1.

[CO1, C2,
Mark: 3]

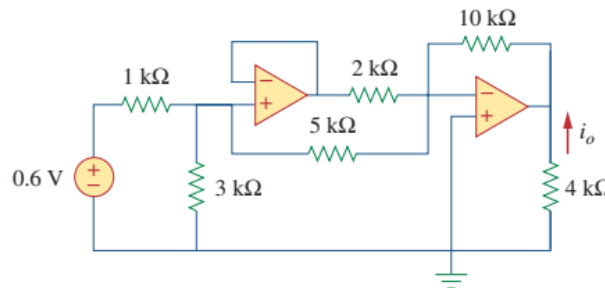


Fig. 1

2. **Design** a circuit such that

$$-v_{out} = -5v_1 + v_2 + 7v_3$$

Let all the resistors be $\leq 100 \text{ K}\Omega$.

[CO3, C4,
EP1,
Mark: 5]

3. For a given output voltage in Fig. 2(a), **determine** the input voltage v_i for the differentiator circuit shown in Fig. 2(b). Here, $R_i = R_f = 1 \text{ Mohm}$ and $C = 1\mu\text{F}$.

[CO3, C3,
EP1, EP2,
Mark: 5]

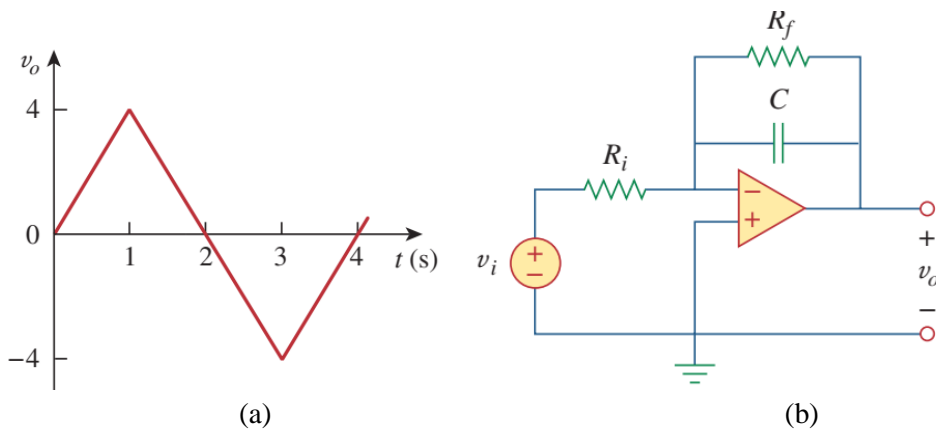


Fig. 2

4. At $t=2$ msec, **determine** the output voltage of the following circuit in Fig. 3. Assume that the integrators are reset to 0 V at $t=0$. [CO3, C4, Mark: 4]

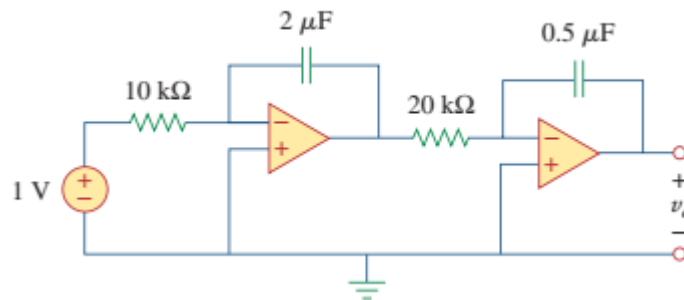


Fig. 3

5. Assuming the op amp to be ideal, it is required to design the circuit shown in Fig. 4 to implement a current amplifier with gain $\frac{i_L}{i_I} = 12$. **Find** the required value for R and R_L if output voltage $v_o = -5$ volt. [CO1, C3, EP1, Mark: 3]

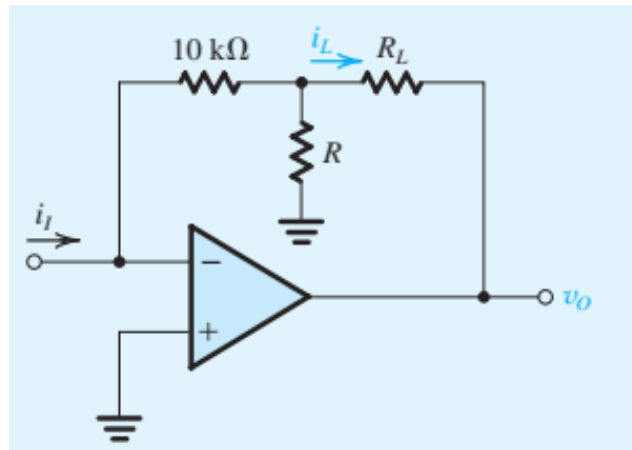


Fig. 4