



EAST WEST UNIVERSITY

Course Title:Electrical Circuits

Course: CSE251

Lab Report (7)

Section:5

Date: 12.1.22

Submitted by:

Student name:Md.Abu Zafor

Student Id:2020-2-60-158

Submitted to:

Touhid Ahmed

Lecturer Department of Computer Science & Engineering


Experiment No: 7

Title: Biasing of a Common-Source Voltage Amplifier.

Objectives:

1. Identify an appropriate DC operation point for a NMOS transistor.

Circuit Diagram:

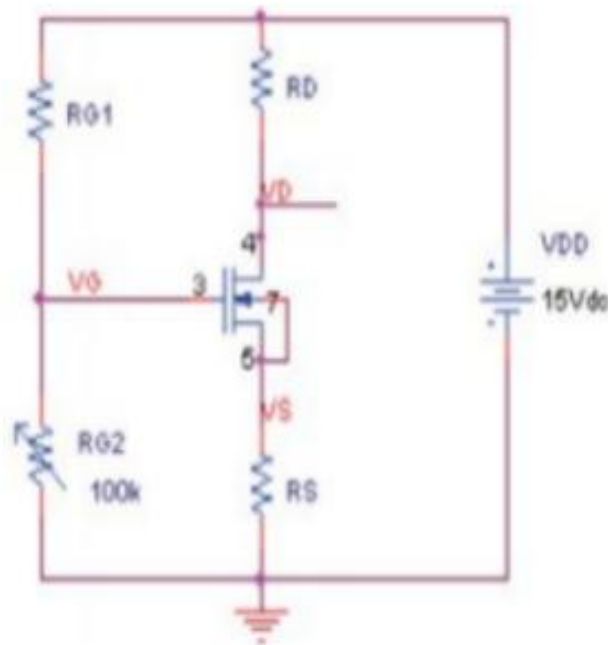

Here,

$I_D = 0.5 \text{ mA}$, $V_{DD} = 15\text{V}$, $V_D = 10\text{V}$, $V_S = 5\text{V}$,

We know,

$$I_D = 0.5 \cdot k_n \cdot V_{ov}^2$$

So, $V_{ov} = 1\text{V}$

$$V_{GS} = V_{ov} + V_{th} = 1 + 1 = 2\text{V}.$$

$$V_G - V_S = 2;$$

$$\therefore V_G = 5 + 2 = 7\text{V}.$$

$$\text{Drain Resistance, } R_D = ((V_{DD} - V_D) / I_D)$$

$$= ((15 - 10) / 0.5) \ \Omega$$


$$= 10 \ \Omega$$

$$\text{Drain Resistance, } R_D = ((V_S - 0) / I_D)$$


$$= ((5 - 0) / 0.5) \ \Omega$$

$$= 10 \ \Omega$$

Circuit of Example:

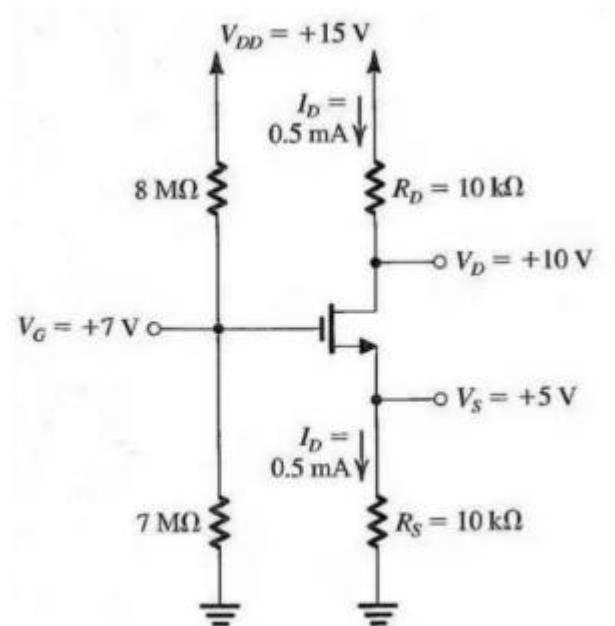

Pspice Simulation:

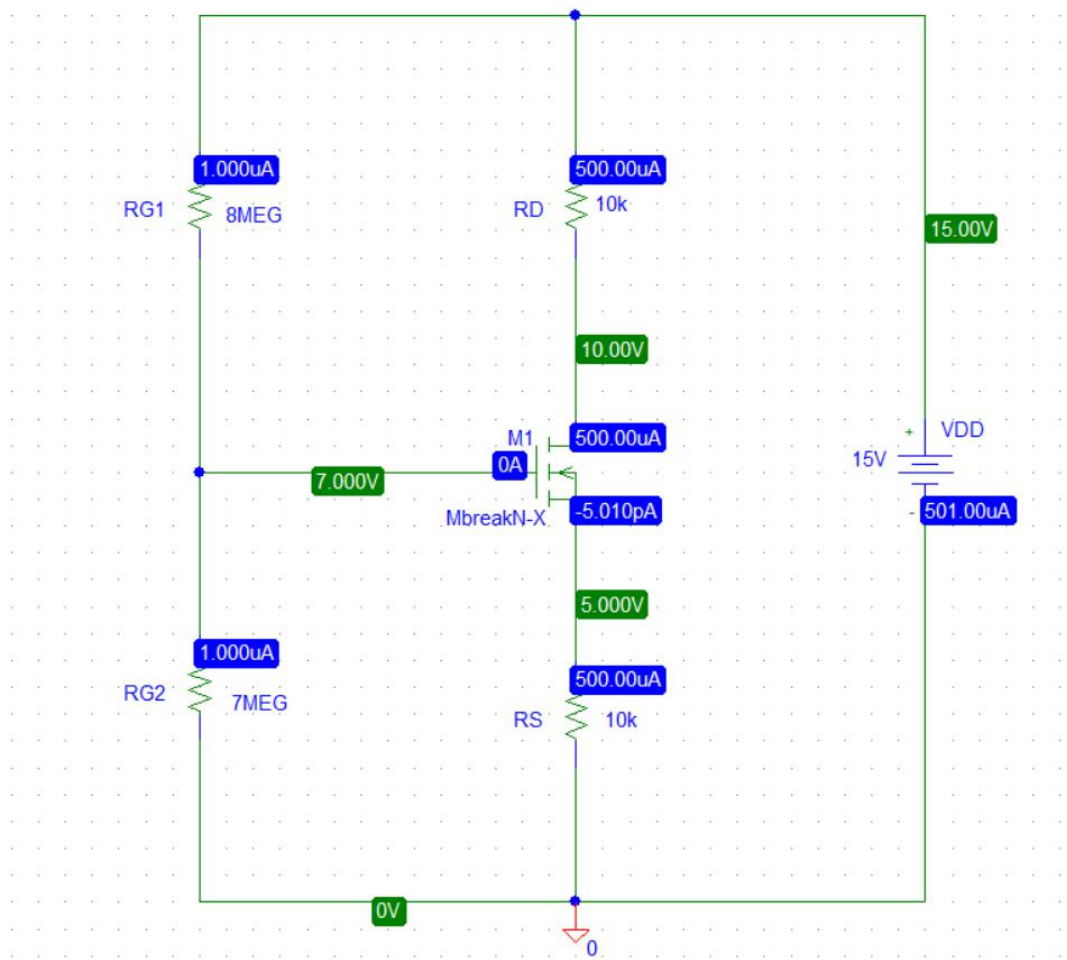

In the Experimental data sheet,

$I_D = 0.6 \text{ mA}$, $V_{DD} = 15\text{V}$, $V_D = 10\text{V}$, $V_S = 4\text{V}$,

We know,

$$I_D = 0.5 \cdot k_n \cdot V_{ov}^2$$

So, $V_{ov} = 1.3\text{V}$

$$V_{GS} = V_{ov} + V_{th} = 1.3 + 1.2 = 2.5\text{V}$$

$$V_G - V_S = 2.5;$$

$$\therefore V_G = 4 + 2.5 = 6.5\text{V}.$$

Drain Resistance, $R_D = ((V_{DD} - V_D) / I_D)$

$$= ((15 - 10) / 0.6) \text{ k}\Omega$$

$$= 8.33 \text{ k}\Omega$$

Drain Resistance, $R_D = ((V_S - 0) / I_D)$

$$= ((4 - 0) / 0.6) \text{ k}\Omega$$

$$= 6.67 \text{ k}\Omega$$

Pspice Simulation:

