

EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Mid Term I Examination, Fall-2021

Course: CSE 251 – Electronic Circuits, Section-5
Instructor: Surajit Das Barman, Senior Lecturer, CSE Department
Full Marks: 20
Time: 1 Hour and 25 Minutes

Note: There are SIX questions, answer ALL of them. Course outcomes (CO), cognitive levels and marks of each question are mentioned at the right margin.

1. **Determine** the value of resistor for a voltage regulator circuit in Fig. 1, where each of diode D_1 and D_2 has a voltage drop of 0.7 V at a current of 10 mA. The analysis should include the operating conditions of the diodes. [CO1, C2, Mark: 3]

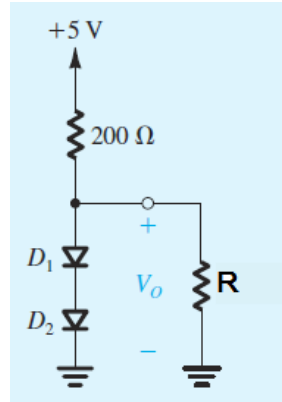


Fig. 1

2. For the input voltage $v_i = 100 \sin \omega t$ and the network in Fig. 2, **sketch** the output voltage v_o and also **calculate** the average value of the output voltage. [CO2, C3, EP1, Mark: 3]

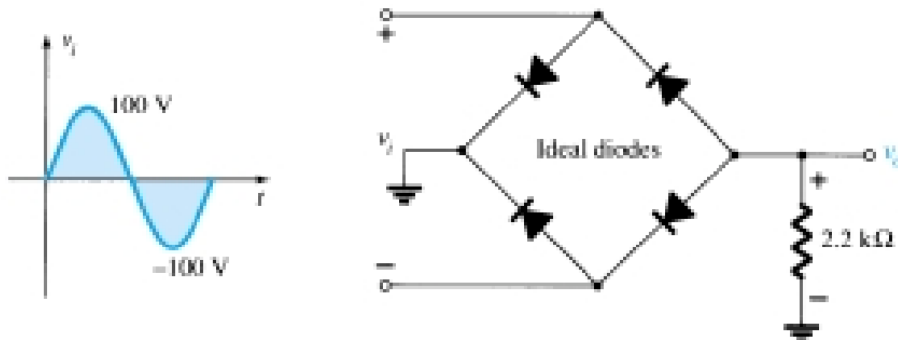


Fig. 2

3. **Sketch** the waveform of output v_o for the network in Fig. 3. Assume, the input voltage v_i is a pure triangular signal having peak-to-peak 24 V and the diodes are silicon diodes. [CO2, C4, EP1, Mark: 5]

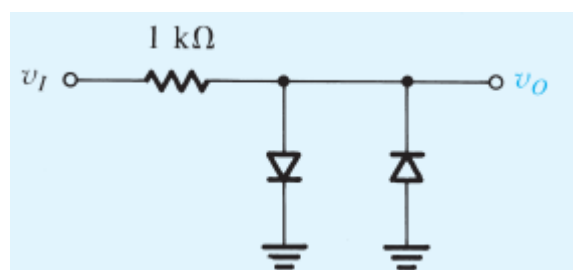


Fig. 3

4. Assuming that the diodes in the circuits of Fig. 4 are ideal, **find** the values of the labeled voltages and currents.

[CO1,
C3, EP1,
Mark: 3]

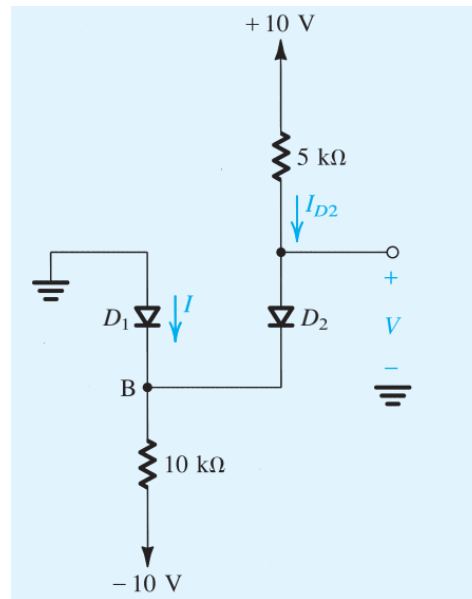


Fig. 4

5. Let $i_C = 2\text{mA}$, $v_{BE} = 0.7\text{V}$ and $\alpha = 0.8$ for a *npn* transistor. **Determine** the value of I_S , i_B , i_E and β .
6. **Design** the circuit in Fig. 5 to establish a current of 0.5mA in the emitter and a voltage of -0.5V at the collector. The transistor $v_{EB} = 0.64\text{V}$ at $I_E = 0.1\text{mA}$ and $\beta = 100$.

[CO1,
C2,
Mark: 2]
[CO2,
C4, EP1,
Mark: 4]

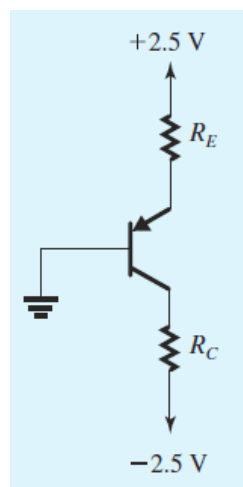


Fig. 5